

Week 4 - T1 2020

# Sequential Circuits Elements and Analysis

ELEC2141: Digital Circuit Design

# Summary

Circuit design

Hierarchical design

Decoders

Encoders

Multiplexers

Demultiplexers

# Overview

Sequential circuits

Latches


Flip- flops

Sequential circuit analysis

**Reading: Mano - Chapter 4, 4.1-4.4**
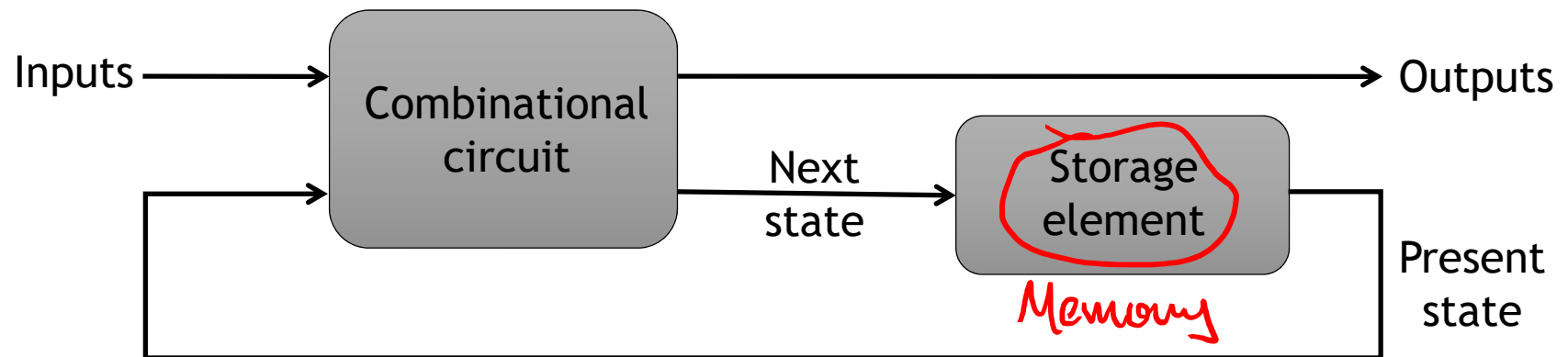
# Sequential circuits

Digital circuits that include storage elements are described as *sequential circuits*




Sequential circuits consist of a combinational circuit connected to storage elements to form a feedback path

Storage elements are devices capable of storing binary data
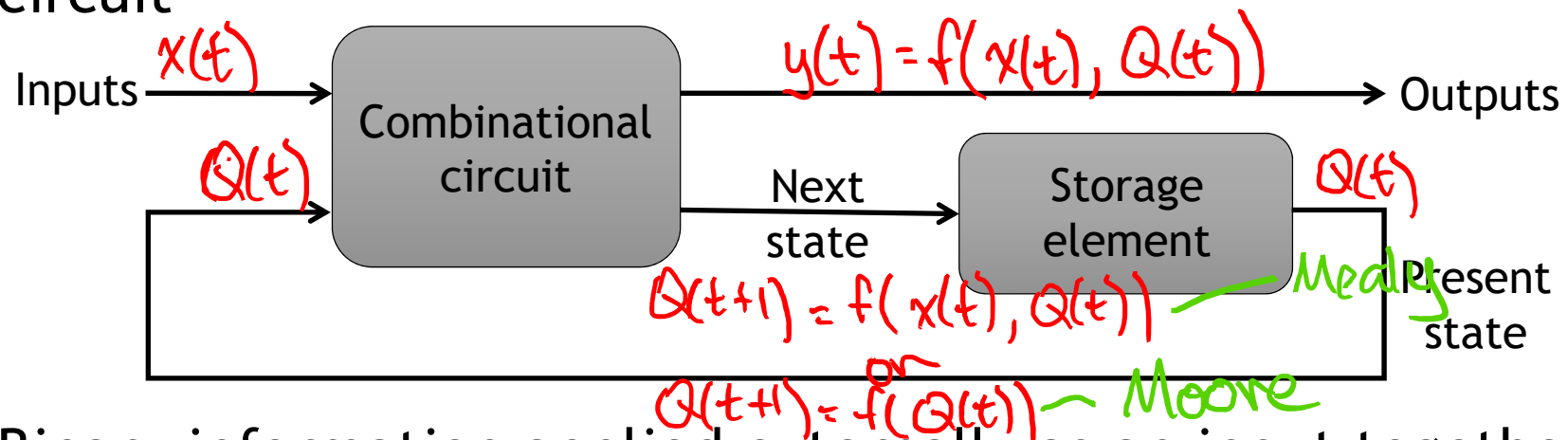
# Sequential circuits

Binary information stored in the storage element at any given time defines the *present state* of the sequential circuit




Binary information applied externally as an input together with the *present state* determines the *next state* of the sequential circuit

The output is also determined by the input and the present state of the sequential circuit
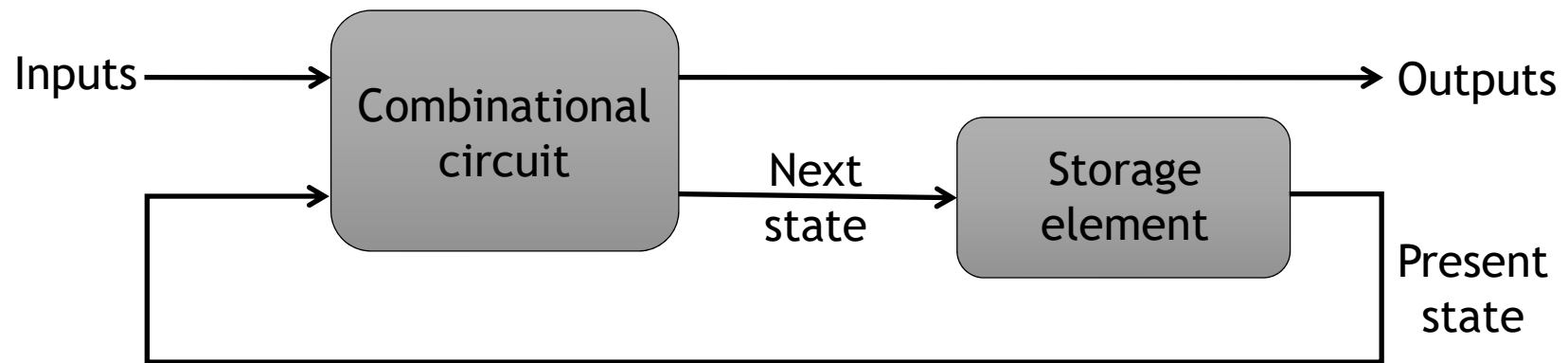
# Sequential circuits

The behavior of the sequential circuit is specified by a time sequence of its inputs, internal states and outputs



Sequential circuits are divided into *synchronous* and *asynchronous* sequential circuits. *\ dependant on clock*

In synchronous sequential circuits, the outputs and states are modified (or changed) only at a discrete instants of time.

# Asynchronous sequential circuits

*Dependant on input event*

In asynchronous sequential circuits, the outputs and states are modified (or changed) only at any instant of time depending upon the inputs

The storage elements commonly used in asynchronous sequential circuits are time delay devices




Propagation delay in a gate or through interconnected gates can constitute a time delay device

Therefore, asynchronous sequential circuits can be regarded as combinational circuits with feedback

The feedback may introduce instabilities at times. The instability problem imposes many difficulties on the designer
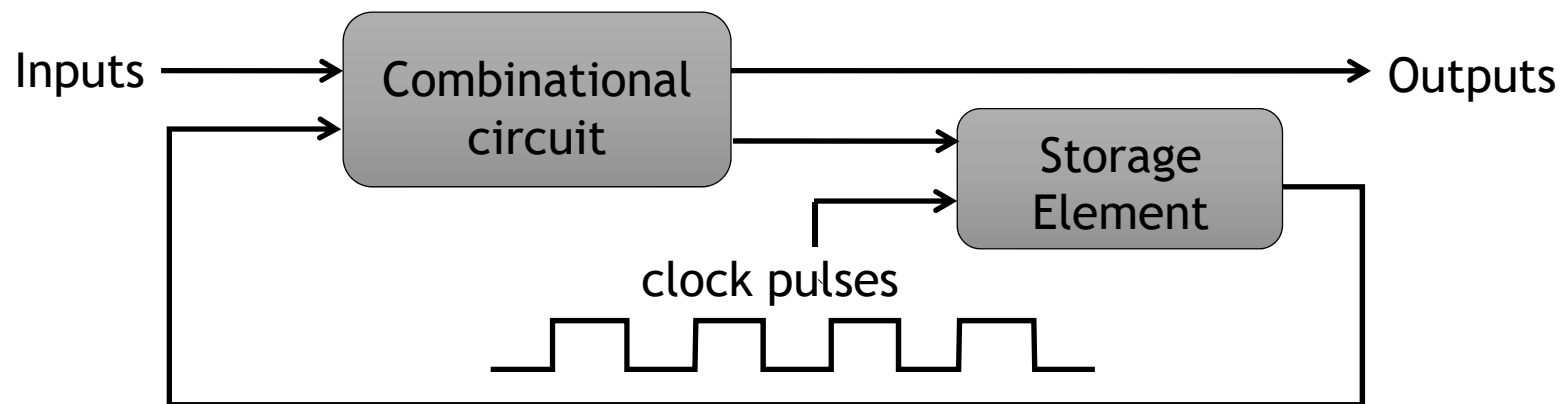
# Synchronous sequential circuits

In synchronous sequential circuits, synchronization is achieved by a timing device called a clock generator.



A clock generator provides a clock signal in the form of periodic train of pulses called clock or clk


Synchronous sequential circuits are also called clocked sequential circuits

They are commonly used as they do not manifest instability and easy to design


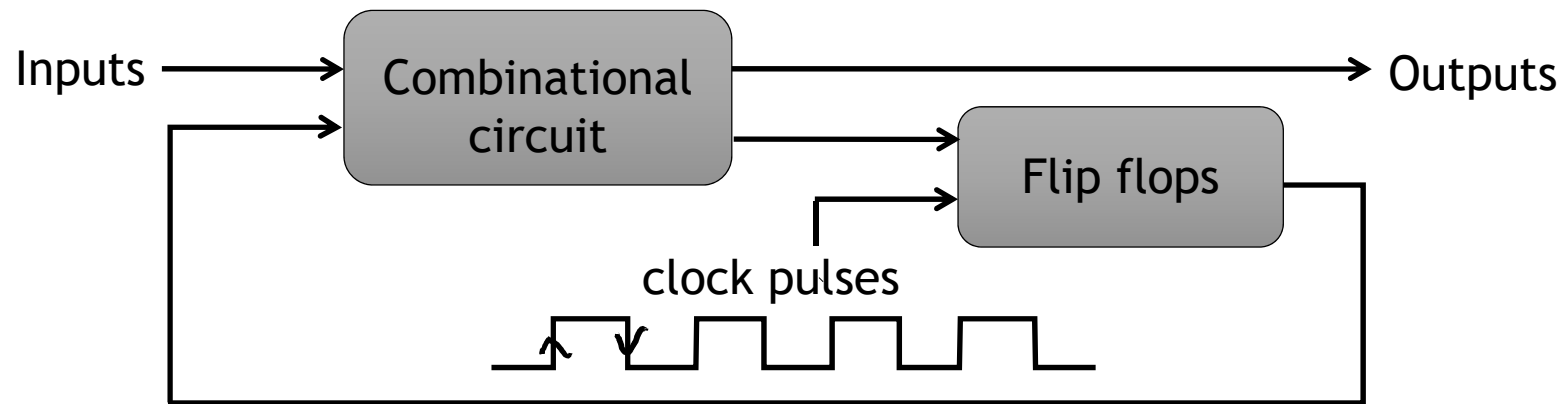
# Synchronous sequential circuits

The storage elements used in clocked sequential circuits are called flip-flops



A flip-flop is a binary storage device that is capable of storing one bit of information

Flip-flops change states only in response to a clock pulse

A flip-flop has two outputs: normal and its complement


$Q$ ,  $\bar{Q}$

# Storage elements

Storage elements are characterized by


- the number of inputs they possess
- the manner in which the inputs affect the binary state

 **Latches** are storage elements that operate based on signal levels and are thus signal level sensitive devices



async.

 **Flip-flops** are storage elements controlled by a clock transition and thus are edge sensitive devices




sync.



UNSW  
SYDNEY

# set/Reset SR latch

 

S	R	Q	$\bar{Q}$	
1	0	1	0	Set
0	0	1	0	
0	1	0	1	Reset
0	0	0	1	
1	1	0	0	Undefined

X	Y	NOR
0	0	1
0	1	0
1	0	0
1	1	0

The **SR latch** is constructed with two cross-coupled NOR gates and two inputs labeled as *S* (set) and *R* (reset)

The latch has two states. When  $Q = 1$  and  $\bar{Q} = 0$ , the latch is said to be in the set state


When  $Q = 0$  and  $\bar{Q} = 1$ , the latch is said to be in the reset state




UNSW  
SYDNEY

# SR latch


X	Y	NOR
0	0	1
0	1	0
1	0	0
1	1	0

 

	S	R	Q	$\bar{Q}$	
→	1	0	1	0	Set
↓	0	0	1	0	
→	0	1	0	1	Reset
↓	0	0	0	1	
	1	1	0	0	Undefined
12	0	0	X	X	Race Condition

 
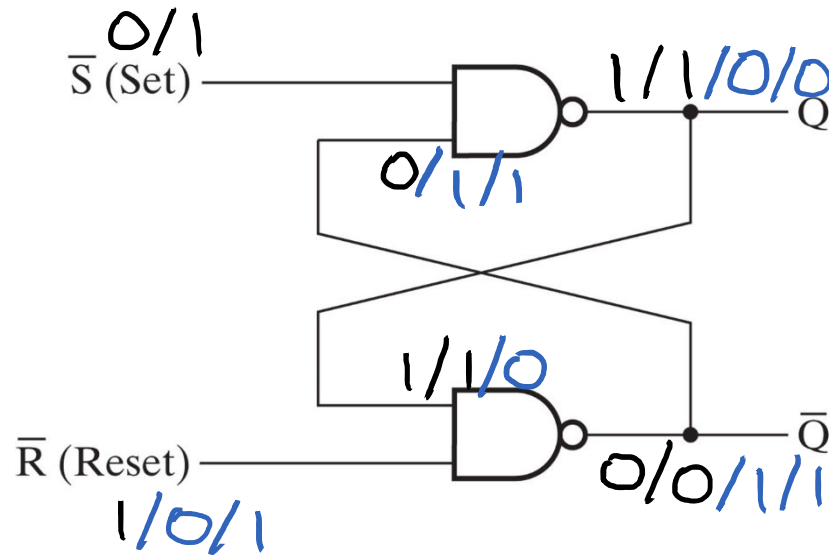
# $\overline{S}\overline{R}$ latch <sup>NAND</sup> active low $\overline{S}\overline{R}$ latch



$\overline{S}$	$\overline{R}$	$Q$	$\overline{Q}$	
0	1	1	0	Set
1	1	1	0	
1	0	0	1	Reset
1	1	0	1	
0	0	1	1	Undefined
1	1	X	X	Race Condition

X	Y	NAND
0	0	1
0	1	1
1	0	1
1	1	0

It can also be constructed with two cross-coupled NAND gates and two inputs labeled  $\overline{S}$  (set) and  $\overline{R}$  (reset).

The latch has two states. When  $Q = 1$  and  $\overline{Q} = 0$ , the latch is said to be in the set state.


When  $Q = 0$  and  $\overline{Q} = 1$ , the latch is said to be in the reset state.



# SR latch with control

Handwritten truth table for NAND inputs:

S	R	NAND
0	0	1
0	1	1
1	0	1
1	1	0

 

<i>En</i>	<i>S</i>	<i>R</i>	Next state of <i>Q</i>
0	X	X	<i>Q</i> unchanged
1	0	0	<i>Q</i> unchanged
1	0	1	<i>Q</i> = 0 Reset
1	1	0	<i>Q</i> = 1 Set
1	1	1	Undefined

The basic operation of SR latch can be modified by adding an enable input signal that determines when the state of the latch can be changed


It consists of the basic SR latch and two additional NAND gates

With  $En = 1$ ,  $S = 1$ , and  $R = 1$  the next state of indeterminate condition occurs




UNSW  
SYDNEY


# SR latch with control

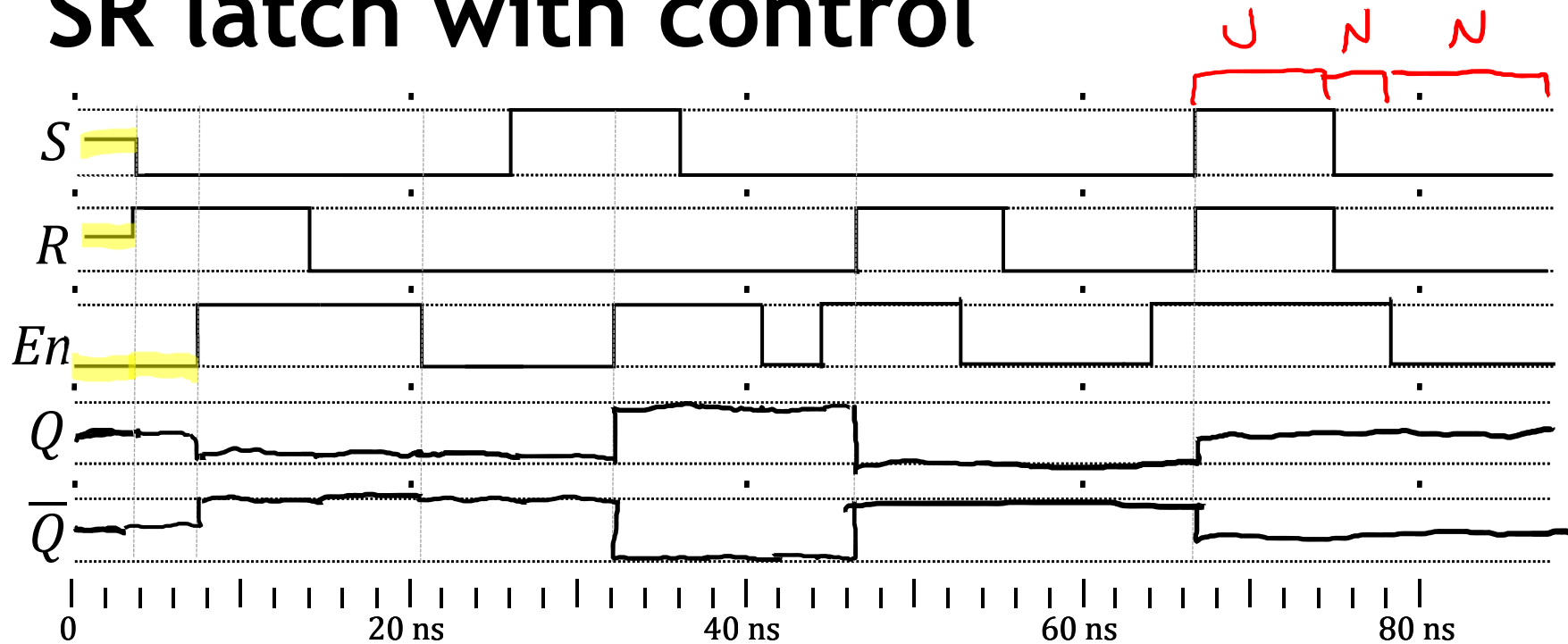

$En$	$S$	$R$	Next state of Q
0	X	X	No change
1	0	0	No change
1	0	1	Q=0 Reset
1	1	0	Q=1 Set
1	1	1	Undefined

 

# D latch

 


<i>En</i>	<i>D</i>	<i>Q</i>
0	X	No change
1	0	$Q=0$ Reset
1	1	$Q=1$ Set

If  $D = 1$ , the  $Q$  output goes to 1, placing the circuit in the set state. If  $D = 0$ , the  $Q$  output goes to 0, placing the circuit in the reset state

The binary information present at the data input of the **D latch** is transferred to the  $Q$  output when the enable input is asserted



# D latch

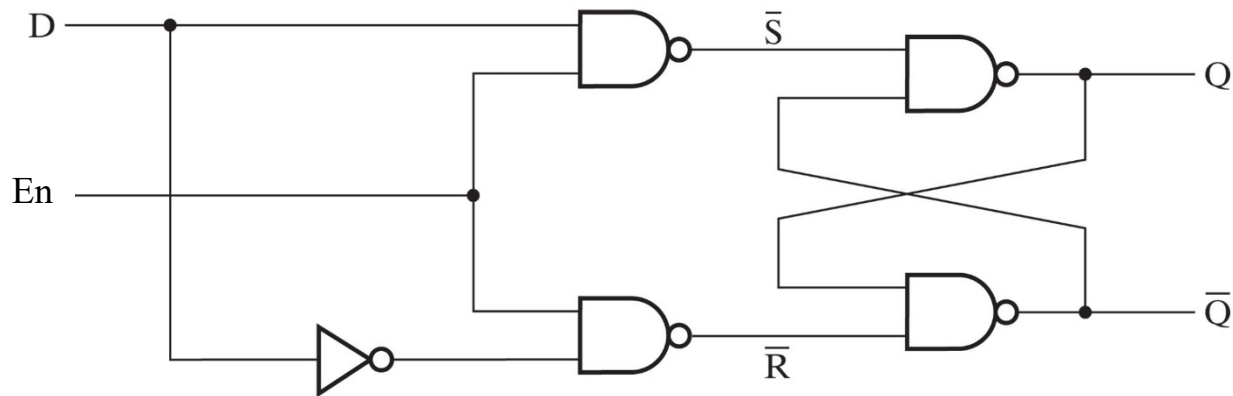

<i>En</i>	<i>D</i>	<i>Q</i>
0	X	No change
1	0	Q=0 Reset
1	1	Q=1 Set


The indeterminate condition in the SR latch when  $En = 1$ ,  $S = 1$ , and  $R = 1$  can be eliminated by ensuring that inputs  $S$  and  $R$  are never equal to 1 at the same time

This is done with a D latch


$En = 0$  produces  $\bar{S} = 1$  and  $\bar{R} = 1$ , which drives the basic SR latch to remain in same state

The D-input is sampled when  $En = 1$

# D latch

 


$En$	$D$	$Q$
0	X	No change
1	0	$Q=0$ Reset
1	1	$Q=1$ Set

 

 
# Latch-designations

A latch is designated by a rectangular block with inputs on the left and outputs on the right

One output designates the normal output and the other designates the complement output



SR latch with  
enable

 


D latch

NAND implementation
 
# Clocked D-Latch

In most sequential circuits, the En (control) input is connected to a clock generator

For a clocked D-latch, the output  $Q$  follows the input  $D$  whenever the clock is high




There may be connecting paths between one storage elements to another, or even back to the same element

Can be a problem when using latches

# The latch timing problem

Consider the following circuit:

 


The output  $Y$  will oscillate whenever the clock is high, and will be constant when the clock is low

Desired behaviour:  $Y$  changes only once per clock pulse
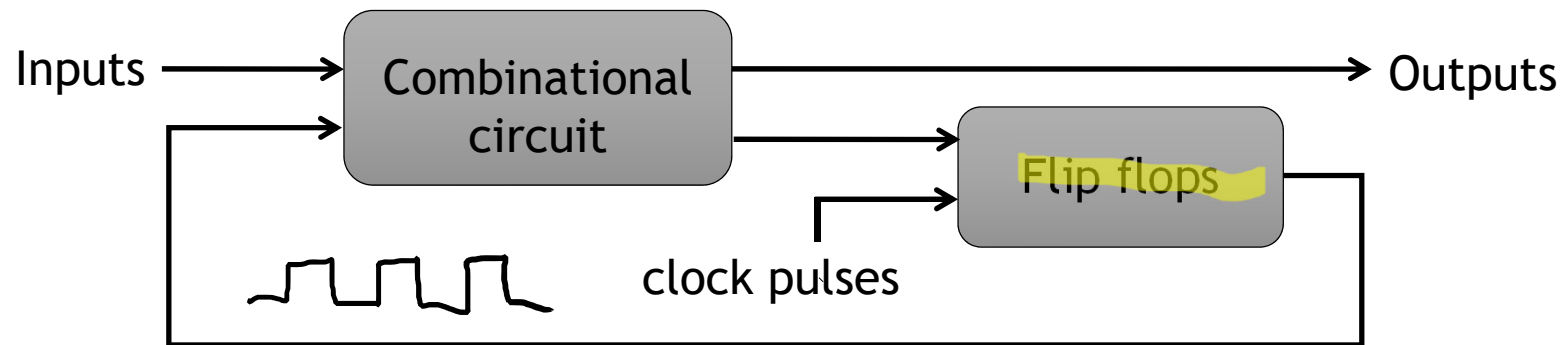
# The latch timing problem


Using latches as storage elements in a synchronous logic circuit will lead to a serious malfunction as the state of the storage element will continue to change as long as the input changes while the clk is high

It is thus difficult to get a stable output when latches are used as storage elements




This can be resolved with *flip-flops* whose states can only change in response to signal transition rather than signal level, i.e. edge sensitive devices

# Solving the timing problem

 
 
# Edge-triggered D flip-flop

A D flip-flop is constructed from two D latches and an inverter



When  $clk = 1$ , master D latch will be enabled while slave D latch is disabled,  $Y = D$

When  $clk = 0$ , master D latch is disabled while slave D latch is enabled,  $Q = D$



This output remains unchanged until the clock transitions from 1 to 0, i.e. it is negative edge triggered



# Edge-triggered D flip-flop

Negative


Clk	D	Q
0	X	No change
1	0	Q=0 Reset
1	1	Q=1 Set

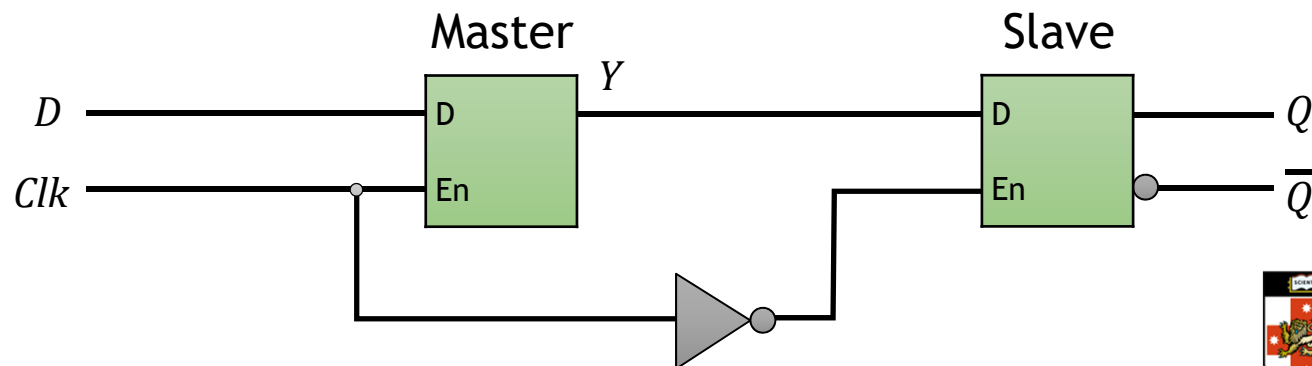 

UNSW  
SYDNEY

# Edge-triggered D flip-flop

In this D flip-flop

 

When  $\text{clk} = 0$ , the master D latch will be enabled while the slave D latch is disabled,  $Y = D$



When  $\text{clk} = 1$ , the master D latch is disabled while the slave D latch is enabled,  $Q = D$

This output remains unchanged until the clock transitions from 0 to 1, i.e. it is positive-edge triggered

# Edge-triggered D flip-flop

positive


Clk	D	Q
0	X	No change
1	0	Q=0 Reset
1	1	Q=1 Set

  


UNSW  
SYDNEY
 
# Flip-flop symbols

Positive and negative edge-triggered D flip-flops are represented by





┐ Triggered  
*positive*

 

┘ Triggered  
*negative*

The symbols  $\lrcorner$  and  $\llcorner$  are used to denote positive and negative edge triggering, respectively

# Level vs Edge Triggered Devices

 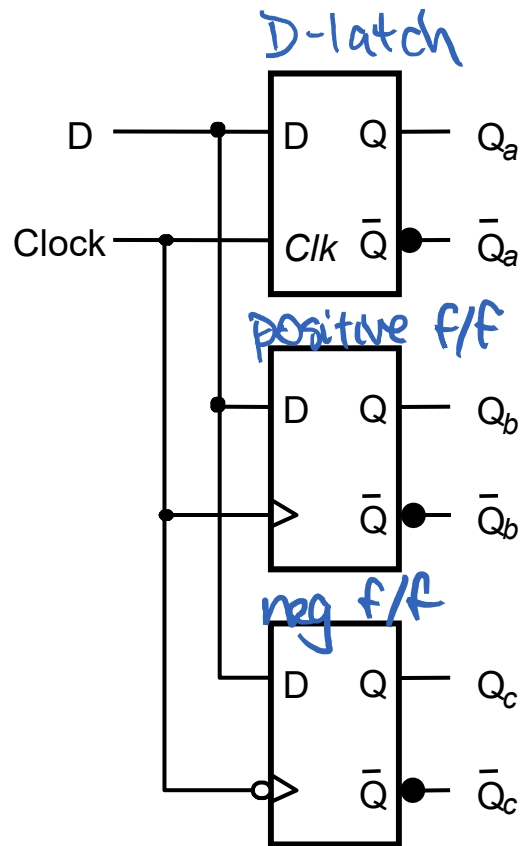


# Direct inputs

Asynchronous *Set* and *Reset* input signals

Used to force a value to the output of the flip-flop, independent of the clock

 Usually used to initialize the circuit to known values at system start-up



Active-low  
set and reset

S	R	Clk	D	Q	$\bar{Q}$
0	1	X	X	1	0
1	0	X	X	0	1
0	0	X	X	Undefined	
1	1	↑	0	0	1
1	1	↑	1	1	0



UNSW  
SYDNEY

# Other flip-flops

The edge triggered D flip-flop requires the smallest number of gates and hence is the most economical and efficient flip-flop


Other types of flip-flops can be constructed by using D flip-flop and external logic

The other two flip-flops less widely used in the design of digital systems are JK and T flip-flops

# JK flip-flops

The JK flip-flop has a similar behavior to the SR latch with the exception that 1-1 input is allowed.


It is built from a D flip-flop, where

 

$J$	$K$	$Q(t+1)$
0	0	$Q(t)$
0	1	0
1	0	1
1	1	$\bar{Q}(t)$



# JK flip-flop

 

$J$	$K$	$Q(t+1)$
0	0	$Q(t)$
0	1	0
1	0	1
1	1	$\bar{Q}(t)$


# T flip-flops

The T (Toggle) flip-flop maintains its stored value when  $T = 0$ , and complements it when  $T = 1$ .


It is built from a D flip-flop, where

$$D = T\bar{Q} + \bar{T}Q$$

$T$	$Q(t+1)$
0	$Q(t)$
1	$\bar{Q}(t)$

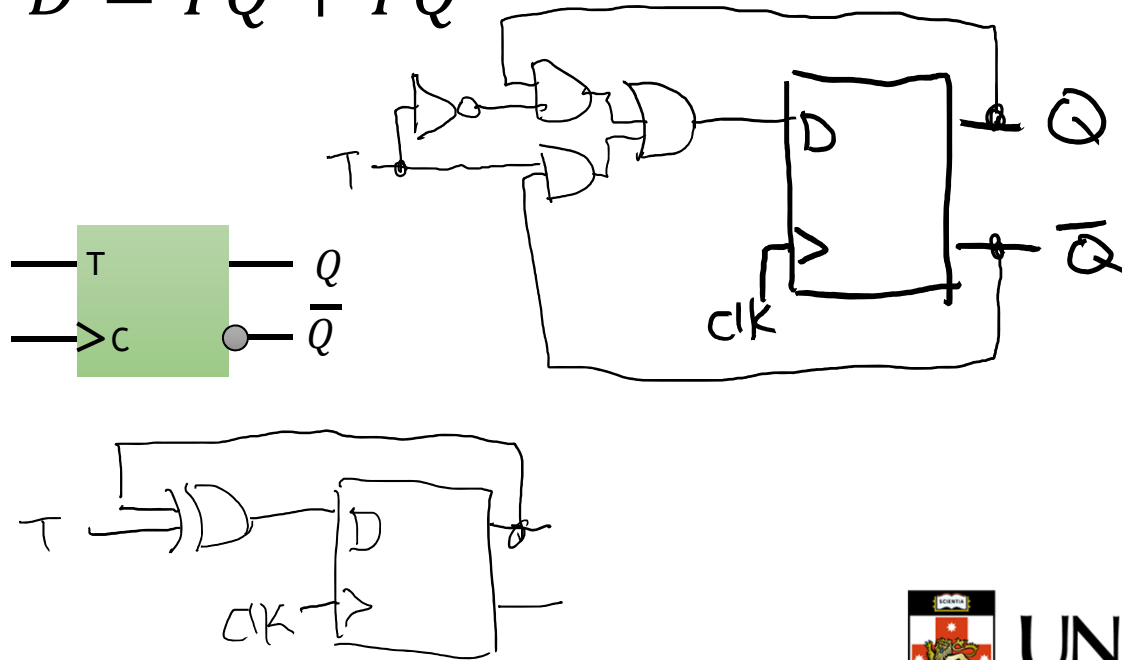

# T flip-flop

 

$T$	$Q(t+1)$
0	$Q(t)$
1	$\overline{Q}(t)$



# Characteristic tables

A characteristic table defines the logical properties of a flip-flop by describing its operation in tabular form.

It defines the next state as a function of the inputs and the presents state.  $Q(t+1) = f(x(t), Q(t))$

The next state is the state of the flip-flop after the clock transition and denoted by  $Q(t+1)$ . *input* *present state*

The present state is the state of the flip-flop immediately before the clock edge and denoted by  $Q(t)$ .

# Characteristic tables

$J$	$K$	$Q(t+1)$	
0	0	$Q(t)$	unchanged
0	1	0	Reset
1	0	1	Set
1	1	$\overline{Q}(t)$	Complement

$D$	$Q(t+1)$	
0	0	Reset
1	1	Set

$T$	$Q(t+1)$	
0	$Q(t)$	unchanged
1	$\overline{Q}(t)$	toggle / complement.

# Characteristic equations

Present			Next
Q	J	K	$Q(t+1)$
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	0

$Q(t+1)$ :

Q \ JK	J			
	00	01	11	10
0	0	0	1	1
1	1	0	0	1

$$Q(t+1) = J\bar{Q} + \bar{K}Q$$

J	K	$Q(t+1)$
0	0	$Q(t)$
0	1	0
1	0	1
1	1	$\bar{Q}(t)$



UNSW  
SYDNEY

# Characteristic equations

$Q$	$D$	$Q(t+1)$
0	0	0
0	1	1
1	0	0
1	1	1

Reset

Set

Reset

Set

$Q(t+1):$

$Q \backslash D$	0	1
0	0	1
1	0	1

$$Q(t+1) = D$$

$Q$	$T$	$Q(t+1)$
0	0	0
0	1	1
1	0	1
1	1	0

unchanged

toggle

unchanged

toggle

$Q(t+1):$


$Q \backslash T$	0	1
0	0	1
1	1	0

$$Q(t+1) = \overline{T}Q + T\overline{Q}$$

$$= T \oplus Q$$
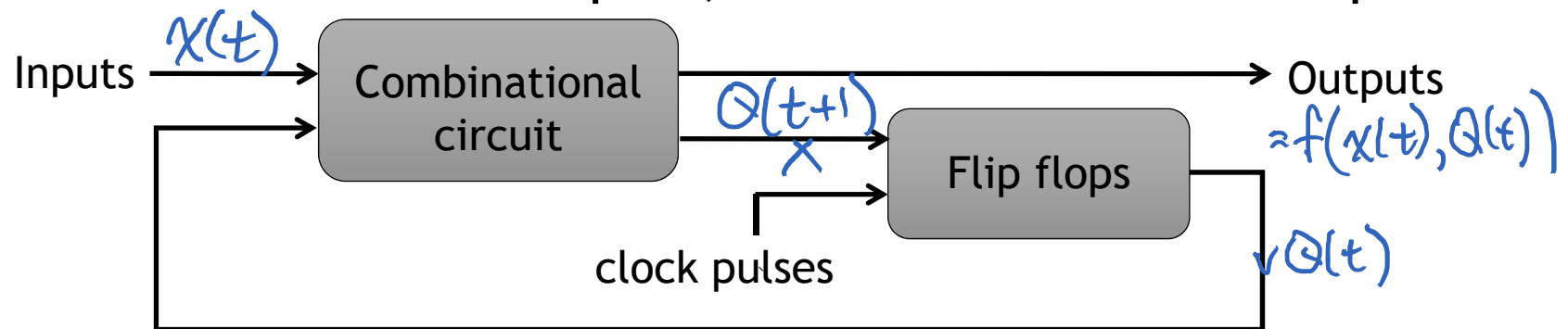
# Analysis of clocked sequential circuits

The behavior of a clocked sequential circuit is determined from the inputs, internal states and outputs.



The outputs and the next state are both a function of the inputs and the present state

Sequential circuit are analysed by obtaining a table or a diagram for the inputs, internal states and outputs

Boolean expressions can then be used to describe the behaviour of the sequential circuit



# Analysis of clocked sequential circuits

State equations, a state table and a state diagram are used to describe the behavior of any clocked sequential circuit


A *state equation* (*transition equation*) specifies the next state as a Boolean function of the present state and inputs

State eqn.  $Q(t+1) = Q(t)x(t) + \bar{Q}(t)(y(t) + x(t))$

logic func.  $W(t) = x(t) + Q(t)y(t)$  - purely comb. Cir.
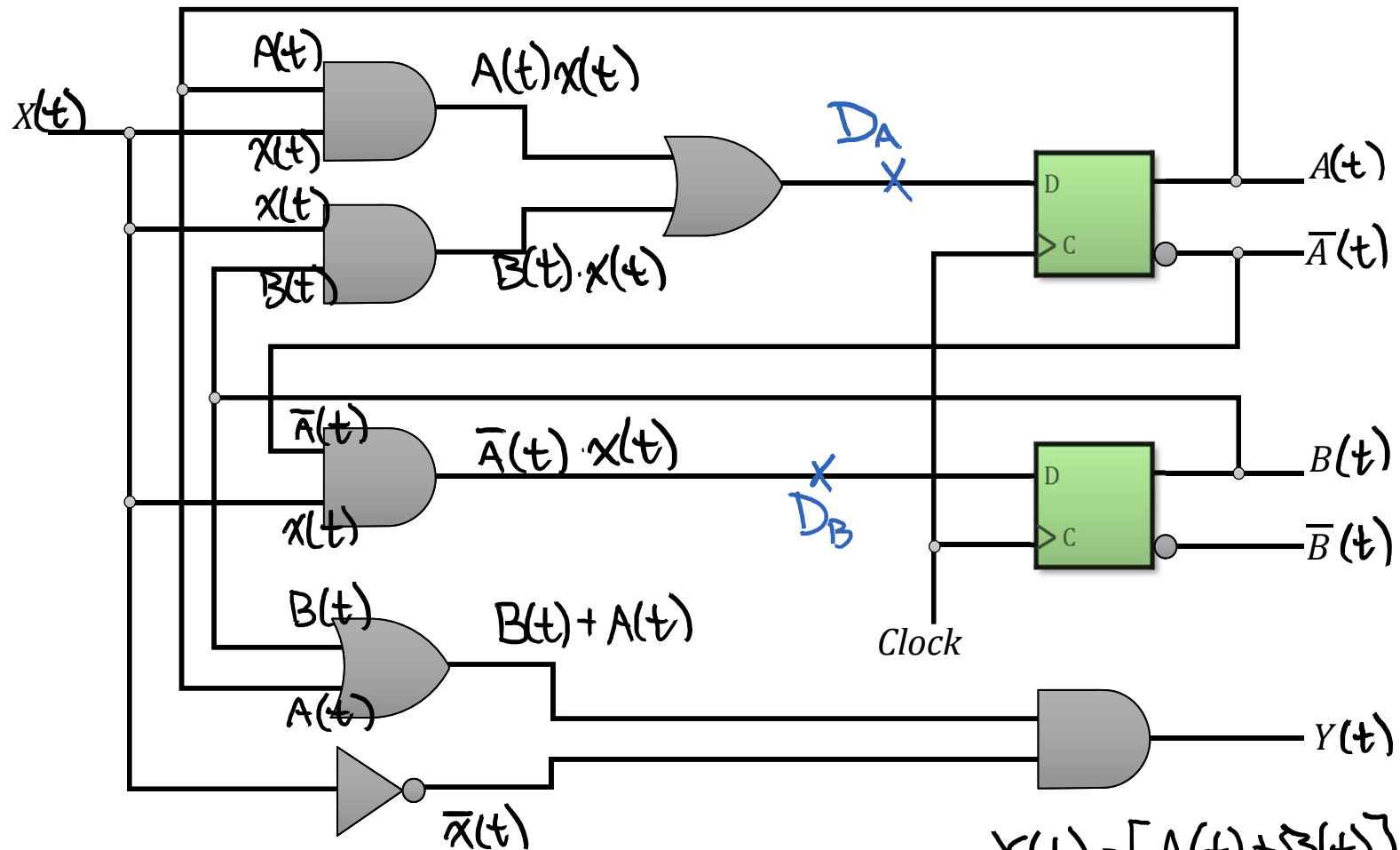
# State equations

$$D_A = A(t+1) = [A(t) + B(t)] \cdot X(t)$$




$$D_B = B(t+1) = \bar{A}(t) \cdot X(t)$$

$$Y(t) = [A(t) + B(t)] \cdot \bar{X}(t)$$



UNSW  
SYDNEY

# State equations

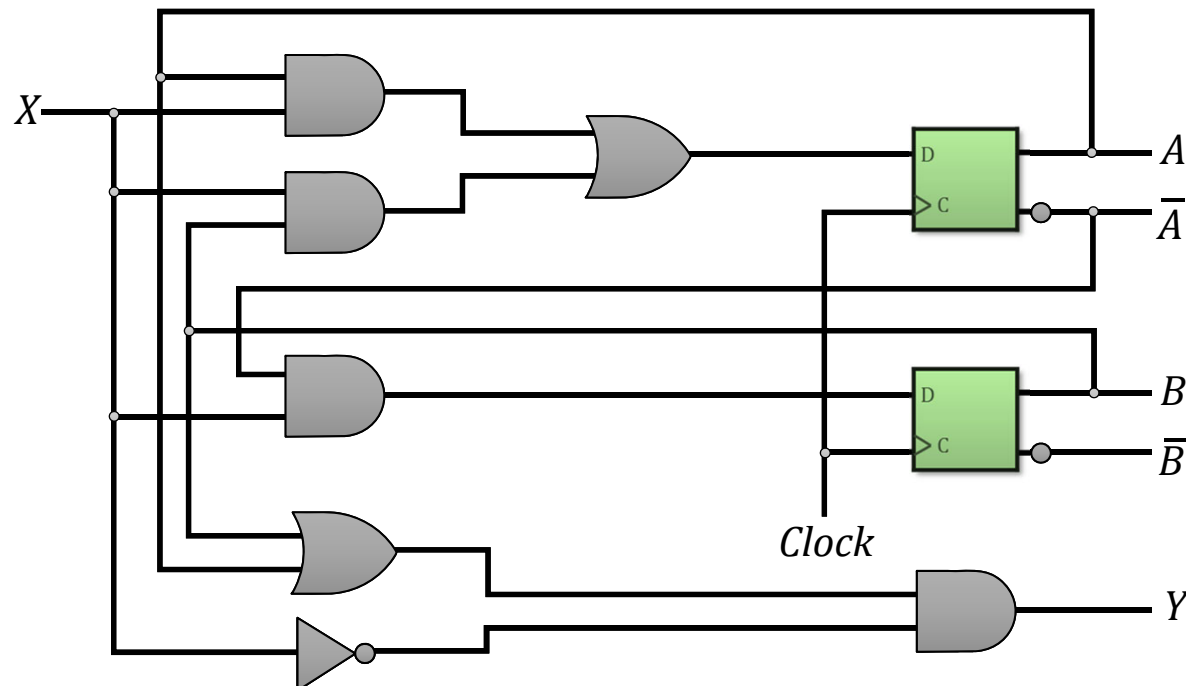

The D input of a flip-flop determines the value of the next state (i.e. the state after the clock transition)

$$A(t + 1) = A(t)x(t) + B(t)x(t)$$

$$B(t + 1) = \bar{A}(t)x(t)$$

The present-state of the output is given by

$$Y(t) = [A(t) + B(t)]\bar{x}(t)$$

# State Equations

Since all variables in the Boolean expressions are a function of the present state, the designation of  $(t)$  after each variable can be omitted

$$A(t + 1) = Ax + Bx$$

$$B(t + 1) = \bar{A}x$$


The present-state value of the output can be expressed algebraically as

$$Y(t) = [A + B]\bar{x}$$

# Problem

$$A(t+1) = D_A = W\bar{A} + \bar{A}B$$

$$B(t+1) = D_B = \bar{A}B + A\bar{B}$$

 

$$X(t) = AB$$

$$Y(t) = \bar{A}B$$

$$Z(t) = A\bar{B}$$

# State table

It is possible to enumerate the time sequences of inputs, outputs and states of the sequential circuit using a *state table* (*transition table*)

The table consists of four sections labelled present state, input, next state and output

The derivation of a state table requires listing all possible binary combinations of present states and inputs

The next-states and the output values are then determined from the logic diagram or state equations for each possible binary combination

# State table

$(t)$ 

 $\downarrow$   
 $(t+1)$

Present state		Input	Next state		Output
<i>A</i>	<i>B</i>	<i>X</i>	<i>A</i>	<i>B</i>	<i>Y</i>
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	0	1
0	1	1	1	1	0
1	0	0	0	0	1
1	0	1	1	0	0
1	1	0	0	0	1
1	1	1	1	0	0

$$\begin{aligned} \rightarrow A(t+1) &= \downarrow A x + \downarrow B x \\ \rightarrow B(t+1) &= \bar{A} x \\ Y(t) &= [A + B] \bar{x} \end{aligned}$$

# State table

The state transition can be conveniently expressed in a slightly different form having only three sections: present state, next state and output

Present state	Next state				Output	
	input $X=0$		input $X=1$		$X=0$	$X=1$
$A \ B$	$A$	$B$	$A$	$B$		
0 0	0	0	0	1	0	0
0 1	0	0	1	1	1	0
1 0	0	0	1	0	1	0
1 1	0	0	1	0	1	0

$$A(t + 1) = Ax + Bx$$

$$B(t + 1) = \bar{A}x$$

$$Y(t) = [A + B]\bar{x}$$



# Problem


$$A(t + 1) = \bar{A}w + \bar{A}B$$

$$B(t + 1) = A\bar{B} + \bar{A}B$$

$$X(t) = AB$$

$$Y(t) = \bar{A}B$$


$$Z(t) = A\bar{B}$$

 

Present state		Next state				Output		
						X	Y	Z
		w=0		w=1				
A	B	A	B	A	B			
0	0	0	0	1	0	0	0	0
0	1	1	1	1	1	0	1	0
1	0	0	1	0	1	0	0	1
1	1	0	0	0	0	1	0	0



# State diagram

 


The information available in state tables can be represented graphically in the form of a state diagram

In a state diagram, a state is indicated by a circle and the transitions between the states are represented by directed lines connecting the circles


The directed lines are labeled with two binary numbers separated by a slash

 The first binary number is for the input value and the second number shows the output value for the given input value during the present state which is represented by a circle from which the directed line emanates



# State diagram

Present state	Next state				Output	
	$X=0$		$X=1$		$X=0$	$X=1$
A B	A	B	A	B		
0 0	0	0	0	1	0	0
0 1	0	0	1	1	1	0
1 0	0	0	1	0	1	0
1 1	0	0	1	0	1	0


 


The same information is conveyed by both state diagram and state table.

State diagrams provides pictorial representation that is easier for human representation.

# Problem

Present state		Next state				Output		
						X	Y	Z
		w=0		w=1				
A	B	A	B	A	B			
0	0	0	0	1	0	0	0	0
0	1	1	1	1	1	0	1	0
1	0	0	1	0	1	0	0	1
1	1	0	0	0	0	1	0	0

  


UNSW  
SYDNEY
 
# State and output time sequence

The state table and state diagram can be used to find state and output time sequences

Here for an input sequence of 010100110 assuming the sequential is initially in state 00, the state and outputs are



Present state		Next state				Output	
		X=0		X=1		X=0	X=1
A	B	A	B	A	B		
0	0	0	0	0	1	0	0
0	1	0	0	1	1	1	0
1	0	0	0	1	0	1	0
1	1	0	0	1	0	1	0

X	0	1	0	1	0	0	1	1	0	0
A	0	0	0	0	0	0	0	1	0	0
B	0	1	0	1	0	0	1	1	0	0
Y	0	0	1	0	1	0	0	0	1	0



UNSW  
SYDNEY


# Flip-flop input equations

*Flip-flop equations* are the Boolean functions that describes the part of the sequential circuit that generate the flip flop inputs

$$D_A = Ax + Bx$$

$$D_B = \bar{A}x$$

$$Y = [A + B]\bar{x}$$

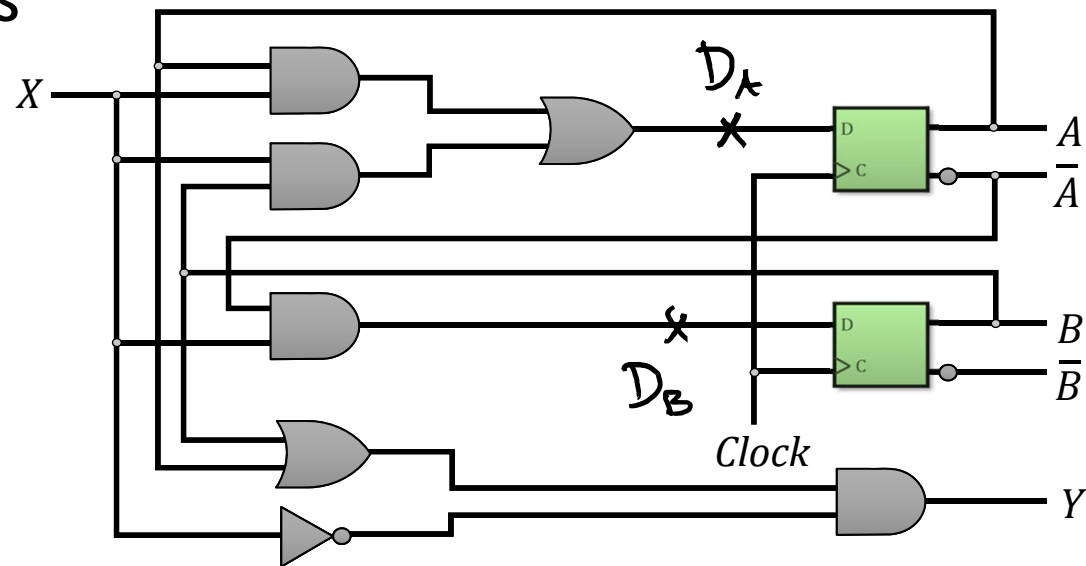

The three equations provide the necessary information for drawing the logic diagram of the sequential circuit


$D_A$  specifies a D flip-flop labeled A and  $D_B$  the D flip-flop labeled B

# Analysis with D flip-flops

Steps in analyzing sequential circuits with D flip-flops:

1. Find the flip-flop input equations
2. The state equations are the same as the flip-flop input equations for D flip-flops
3. Derive the state table from the state equations
4. Draw the state diagram from the state table

Example:


 


# Analysis with D flip-flops

State table:  $t$   $(t+1)$

Present state	Input		Next state
A	X	Y	A
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

State Diagram:

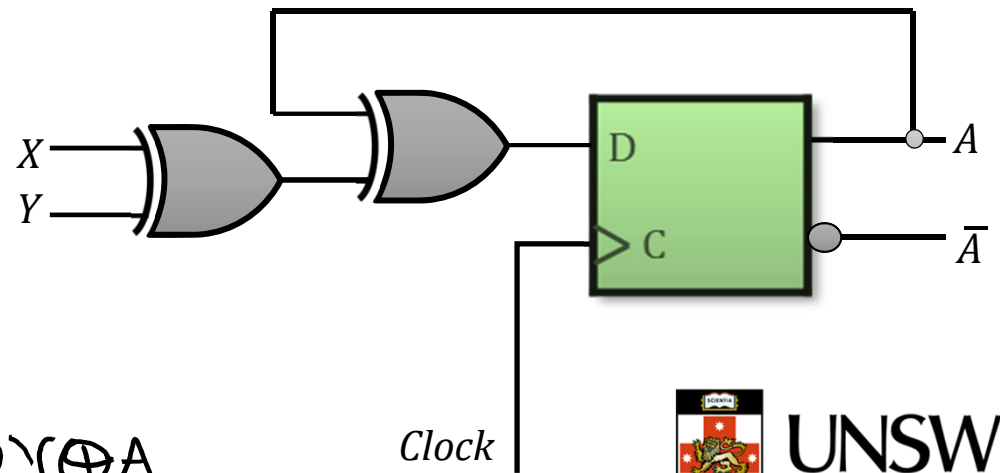 

$$A(t+1) = X \oplus Y \oplus A$$



UNSW  
SYDNEY




# Analysis with JK flip-flops

Steps in analyzing sequential circuits with JK flip-flops:

1. Find the flip-flop input equations in terms of present state and input
2. List the binary values of each input equation
3. Use the JK flip-flop characteristic table to determine the next states in the state table
4. Use K-map to obtain minimized state equations

Example:

 

# Analysis with JK flip-flops

Flip-flop input equations:


$$J_A = B$$

$$J_B = \bar{X}$$


$$K_A = B\bar{X}$$

$$K_B = A \oplus X$$

Present state		Input	Next state		Flip-Flop inputs			
A	B	X	A	B	$J_A$	$K_A$	$J_B$	$K_B$
0	0	0	0	1	0	0	1	0
0	0	1	0	0	0	0	0	1
0	1	0	1	1	1	1	1	0
0	1	1	1	0	1	0	0	1
1	0	0	1	1	0	0	1	0
1	0	1	1	0	0	0	0	1
1	1	0	0	0	1	1	1	0
1	1	1	1	1	1	0	0	1

 

$$A(t+1) = \bar{A}B + A\bar{B} + AX$$

 

$$B(t+1) = \bar{A}\bar{X} + ABX + \bar{B}\bar{X}$$



UNSW  
SYDNEY

# Analysis with JK flip-flops

The steps can also be stated as:

1. Find the flip-flop input equations in terms of present state and inputs
2. Substitute the input equations into the flip-flop characteristic equation to obtain the state equations
3. Use the corresponding state equations to determine the next-values in the state table and state diagrams

In the previous example:

$$\begin{aligned} J_A &= B & K_A &= B\bar{X} \\ J_B &= \bar{X} & K_B &= A \oplus x \end{aligned}$$

The characteristic equations for the JK flip-flop:

$$A(t+1) = J_A \bar{A} + \bar{K}_A A = B\bar{A} + A(\overline{B\bar{X}}) = \bar{A}B + A\bar{B} + AX$$


$$\begin{aligned} B(t+1) &= J_B \bar{B} + \bar{K}_B B = \bar{X}\bar{B} + \overline{A \oplus x} B \\ &= \bar{X}\bar{B} + \bar{A}\bar{x} + ABx \end{aligned}$$



# Analysis with JK flip-flops

Present state			Next state			
			X=0		X=1	
A	B		A	B	A	B
0	0		0	1	0	0
0	1		1	1	1	0
1	0		1	1	1	0
1	1		0	0	1	1

State Diagram:

 

$$A(t+1) = J_A \bar{A} + \bar{K}_A A$$

$$B(t+1) = J_B \bar{B} + \bar{K}_B B$$



UNSW  
SYDNEY

# Analysis with T flip-flops

The same procedure as with JK flip-flops is followed:

1. Find the flip-flop input equations in terms of present state and inputs
2. List the binary values of each input equation
3. Use the T flip-flop characteristic table to determine the next states in the state table
4. Use K-map to obtain minimized state equations

OR

1. Find the flip-flop input equations in terms of present state and inputs
2. Substitute the input equations into the flip-flop characteristic equation to obtain the state equations
3. Use the corresponding state equations to determine the next-values in the state table and state diagrams


# Analysis with T flip-flops

Flip-flop input equations:

$$T_A = Bx \qquad T_B = X$$

Output equation:

$$Y = AB$$

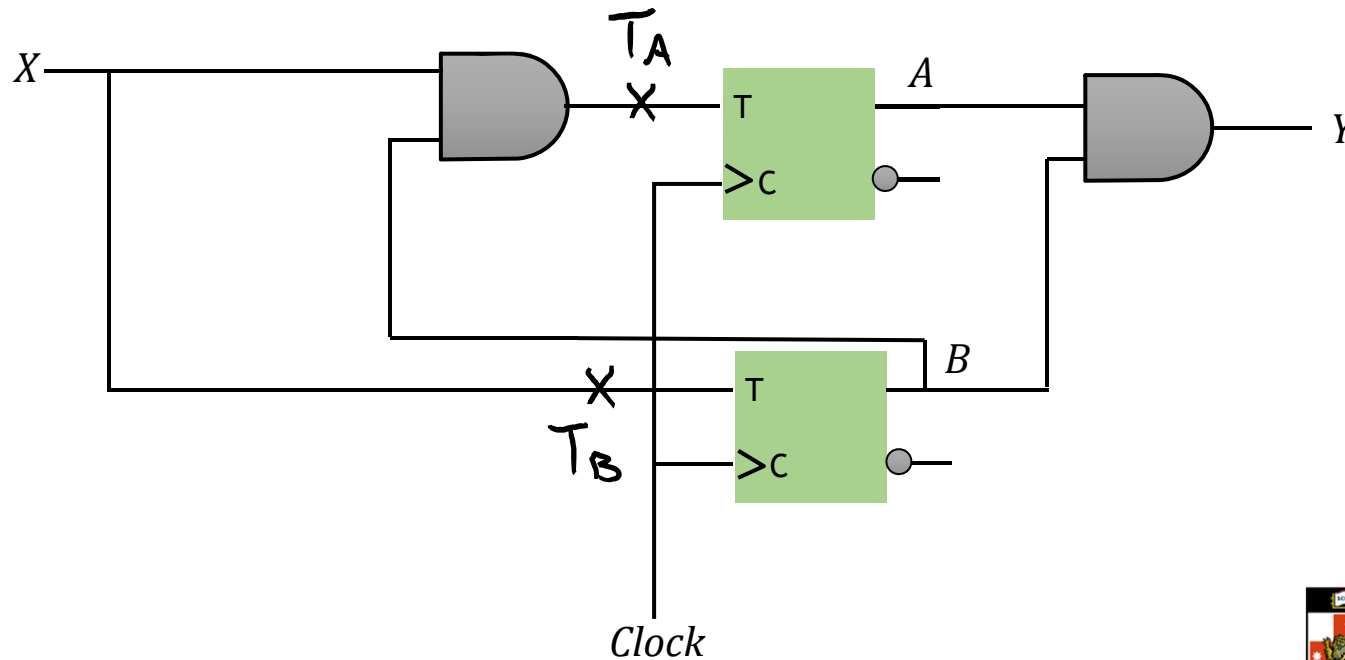


# Analysis with T flip-flops

T	Q(t+1)
0	Q(t)
1	$\overline{Q(t)}$


Present state		Input	Next state		Flip-Flop inputs	
A	B	X	A	B	T <sub>A</sub>	T <sub>B</sub>
0	0	0	0	0	0	0
0	0	1	0	1	0	1
0	1	0	0	1	0	0
0	1	1	1	0	1	1
1	0	0	1	0	0	0
1	0	1	1	1	0	1
1	1	0	1	1	0	0
1	1	1	0	0	1	1

$$T_A = BX \quad T_B = X$$

$$Y = AB$$

 
 
$$A(t+1) = \overline{A}BX + A\overline{B}X + AX$$



$$B(t+1) = \overline{B}X + B\overline{X} = B \oplus X$$



UNSW  
SYDNEY

# Analysis with T flip-flops

Here

$$T_A = BX$$

$$T_B = X$$

Characteristic equation for T flip-flop:

$$A(t + 1) = T_A \oplus A$$

$$B(t + 1) = T_B \oplus B$$



# Analysis with T flip-flops


Present state	Next state				Output	
	$X=0$		$X=1$		$X=0$	$X=1$
$A \ B$	$A$	$B$	$A$	$B$	$Y$	$Y$
0 0	0	0	0	1	0	0
0 1	0	1	1	0	0	0
1 0	1	0	1	1	0	0
1 1	1	1	0	0	1	1

$$A(t+1) = T_A \oplus A$$

$$B(t+1) = T_B \oplus B$$

$$Y = AB$$

State Diagram:

 

UNSW  
SYDNEY